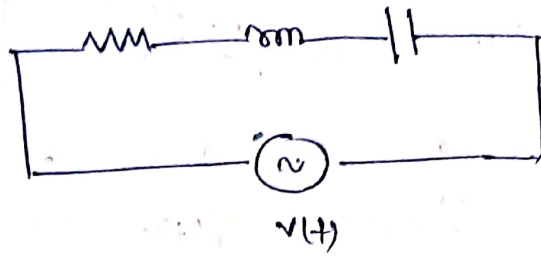



Numericals

Type-1




Series

Type-2

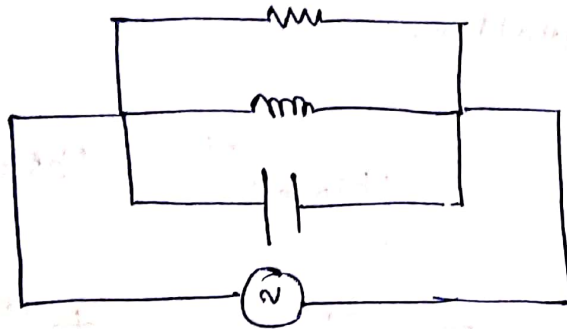

parallel


Type-3

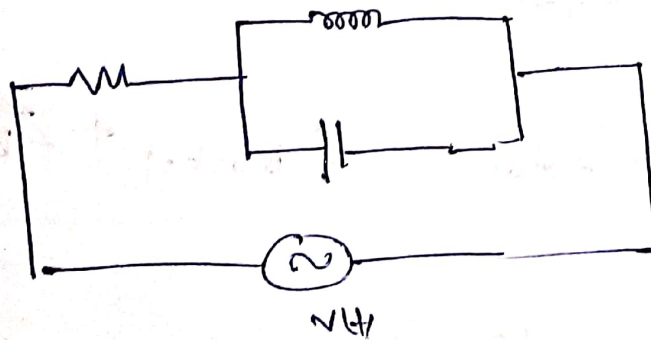

Series parallel


Method is same for any type Question
As Explained in class and Video shared.

Ex: 3. Let us solve type-3. with value.

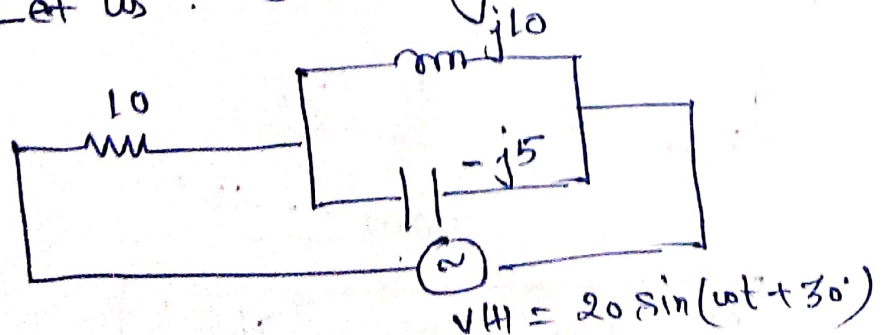

Using current divider
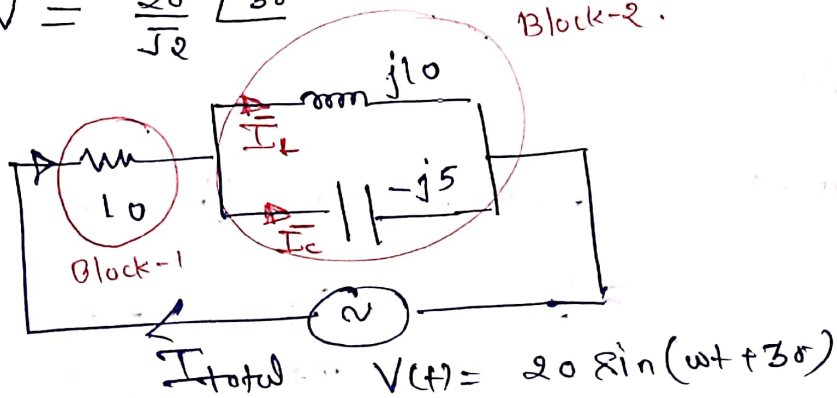
$$\bar{V} = \frac{20}{\sqrt{2}} \angle 30^\circ$$



Master Equation.

$$\bar{V} = V_{Block-1} + V_{Block-2}$$

$$\bar{I} Z_{total} = \bar{I} Z_{Block-1} + \bar{I} Z_{Block-2}$$

$$Z_{total} = Z_{Block-1} + Z_{Block-2}$$

$$= 10 - j10$$

$$= \sqrt{10^2 + 10^2} \angle \tan^{-1} \left[\frac{-10}{10} \right]$$

$$\boxed{\bar{Z}_{total} = \sqrt{200} \angle -45^\circ}$$

$$\bar{I}_{total} = \frac{\frac{20}{\sqrt{2}} \angle 30^\circ}{\sqrt{200} \angle -45^\circ}$$

$$\boxed{\bar{I}_{total} = \frac{20}{\sqrt{2} \sqrt{200}} \angle 75^\circ}$$

$$Z_{Block-1} = 10$$

$$Z_{Block-2} = \frac{j10 \times (-j5)}{j10 - j5}$$

$$= \frac{+50}{j5}$$

$$= \frac{10}{j} = -j10$$

Using current divider

$$\begin{aligned}\bar{I}_L &= \frac{\bar{I}_{total} \cdot \bar{Z}_C}{Z_C + Z_L} \\ &= \frac{\frac{20}{\sqrt{2}} \times 5 \angle 90^\circ \angle 75^\circ}{-j5 + j10}\end{aligned}$$

$$= \frac{100}{\sqrt{2} \sqrt{200}} \angle 165^\circ$$

$$= \frac{100}{\sqrt{2} \sqrt{200}} \frac{\angle 165^\circ}{5 \angle 90^\circ}$$

$$= \frac{20}{\sqrt{2} \sqrt{200}} \angle 165^\circ - 90^\circ$$

$$\boxed{\bar{I}_L = \frac{20}{\sqrt{2} \sqrt{200}} \angle 75^\circ}$$

$$\bar{I}_C = \frac{\bar{I}_{total} \cdot \bar{Z}_L}{Z_L + Z_C}$$

$$= \frac{20}{\sqrt{2} \sqrt{200}} \times \frac{10 \angle 90^\circ}{j5} \times 5 \angle 75^\circ$$

$$= \frac{200 \angle 90^\circ \angle 75^\circ}{\sqrt{2} \sqrt{200} \times 5 \angle 90^\circ}$$

$$= \frac{40 \angle 75^\circ}{\sqrt{2} \sqrt{200}}$$

Amey

Take any Question like type
- 2 and type. 1 also
and solve similar approach
